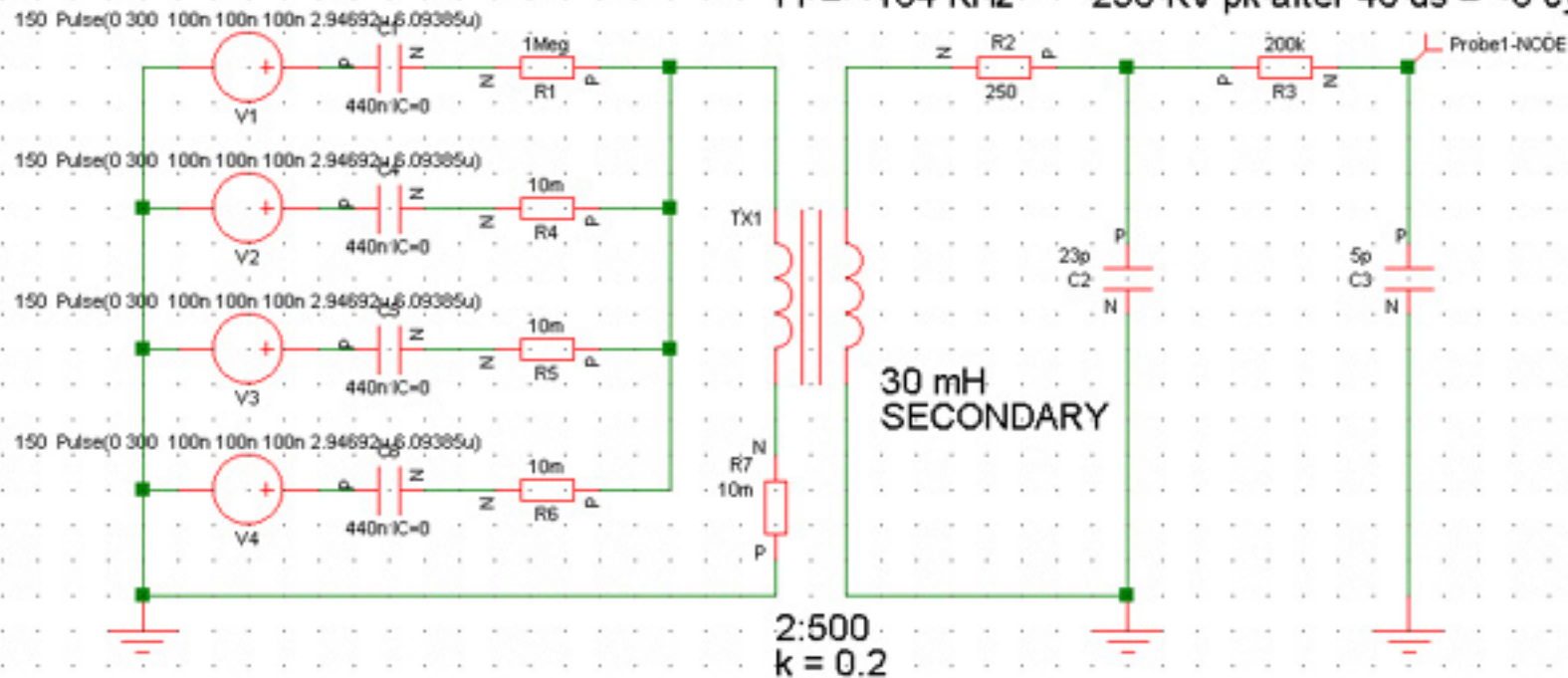


~420 A rms each

$f_r = \sim 164 \text{ KHz}$

250 KV pk after 40 us = ~6 cycles



2 RESONANT PRIMARY-TURNS SIMULATION CIRCUIT

INPUT, 0-300 V SQ. WAVES @ 164 KHz.

KEN HERRICK 5/15/03