

This note describes considerations that should be taken into account when designing a gate drive circuit for an IGBT, and gives some typical circuit suggestions.

When designing a gate drive for an application the following items should be considered:-

- 1) Conduction Losses
- 2) IGBT Switching Losses
- 3) Anti Parallel Diode Switching Losses
- 4) Device Protection
- 5) Drive Circuit Isolation and Control Signal Transmission
- 6) Circuit Layout

## 1.1 CONDUCTION LOSSES

When an IGBT is turned on the collector emitter voltage  $V_{CE}$  is a function of gate emitter voltage  $V_{GE}$ . As  $V_{GE}$  is increased the conduction losses are reduced. It is desirable therefore to increase  $V_{GE}$  to the maximum allowed on the data sheet to minimise the conduction losses, however device manufacturers only guarantee short circuit capability with a  $V_{GE}$  of 15V or less. A typical output characteristic for an IGBT is given fig.1.

 


Fig. 1 Typical output characteristics

## 1.2 IGBT SWITCHING LOSSES

When turning an IGBT on or off the switching losses of the device are affected by the level of  $V_{GE}$  and the Gate Resistance ( $R_g$ ). The effect of increasing  $V_{GE}$  or reducing  $R_g$  is to reduce the delay time, rise time and fall times of the device and hence to reduce the switching losses. Reducing the level of  $V_{GE}$  or increasing  $R_g$  results in increased switching losses, but can reduce Electromagnetic Emissions (EMI). Other factors affecting the switching losses are the anti parallel diode (FWD), circuit inductance, snubbers, device junction temperature, operating voltage and current etc.

 


Fig. 2

## 1.3 ANTI PARALLEL DIODE SWITCHING LOSSES

The reverse recovery and turn on characteristics of the FWD are affected by all the factors mentioned in 1.2, and can therefore be controlled to a certain extent by adjusting the speed of the IGBT. In the event of a diode becoming too snappy in an application, the IGBT turn on can be slowed down, hence reducing the value of  $dI/dt$  applied to the diode and so reducing the diode losses. However, this is at the expense of increasing the IGBT losses. An alternative method of reducing the FWD losses in a bridge configuration is to turn on the IGBT with a reduced  $V_{GE}$ . This limits the peak reverse recovery current,  $I_{rr}$ , of

the FWD in the opposite side of the arm, according to the IGBTs' forward output characteristic, (see fig.1).

#### 1.4 DEVICE PROTECTION CONSIDERATIONS

The majority of IGBT manufacturers guarantee that IGBTs will withstand a short circuit for  $10\mu s$  at 50% of the devices rated voltage, with a  $V_{ge}$  of 15V and a starting temperature of  $<125^{\circ}\text{C}$ . Two different types of short circuit conditions should be considered.

- i) When a device is switched into an already existing short circuit (see fig 3 for typical waveforms).
- ii) When a short circuit appears whilst the device is already conducting (see fig 4).

In the second instance both the voltage and collector current rise very quickly. The rapidly rising  $dv/dt$  coupled with the miller capacitance can increase the effective  $V_{ge}$  seen by the IGBT, further increasing the short circuit current level (see equation [1]). For this reason it is good practice to connect some back-to-back zener diodes directly across the gate emitter terminals to limit the level of  $V_{ge}$  (see fig 5).

$$V_{ge} = C \frac{dv}{dt} * R_g + V_g \quad [1]$$

If the device is switched into an already existing short circuit the  $dv/dt$  problem does not exist, and the miller effect is not considered to be as significant a problem.

If the value of  $R_g$  is increased the rise time of the short circuit current can be increased, reducing the energy loss during the short circuit. At turn off an increased  $R_g$  can slow the devices  $di/dt$  hence reducing over voltages.

When a device experiences a short circuit, the current is limited

 


Fig. 4 Typical waveforms of  $I_c$  and  $V_{ce}$  of IGBT being switched into a short circuit

 


Fig. 5 Showing Zener diodes clamping  $V_{ge}$

 


Fig. 3 Typical  $I_c$  and  $V_{ce}$  waveforms of IGBT being switched into a short circuit

according to the devices transfer characteristic. Assuming a  $V_{ge}$  of 15V the short circuit current can reach values of 3 to 4 times the devices rated forward current.

The fault current can be reduced by reducing  $V_{ge}$ . If the user reduces  $V_{ge}$  to  $<15\text{V}$ , the period of time for which the short circuit can be withstood is increased. This circuit is shown in fig 6.

If a device is being used in an application with a  $V_{ge}$  of  $>15\text{V}$  manufacturers will not guarantee the device will turn off the resulting fault current. The current can increase to levels in excess of 10 times the devices rated current. The user should also be aware that when turning off fault currents the  $di/dt$  is considerably greater than is seen under normal operation and the overshoot voltages due to parasitic inductances are increased.

 


Fig. 6 Schematic showing method of reducing gate drive voltage

#### 1.4-1 THE USE OF NEGATIVE GATE BIAS

In addition to the above considerations it is recommended to use a negative gate bias of -15V when turning off an IGBT during a short circuit. A negative bias of -5V is often recommended as being the minimum negative bias required. A negative bias is essential when turning off a fault current for the following reasons. The threshold voltage  $V_{th}$  reduces by approximately  $10\text{mV}/\text{C}$  junction temperature rise. Under fault conditions the  $V_{th}$  can be as much as 2V below the  $25^\circ\text{C}$  figure quoted on the data sheet. Also inherent parasitic and mutual inductance within the IGBT module can introduce a further reduction in the turn off voltage seen by the individual IGBT chips in the module, (see fig 7).

The negative bias is also useful for minimising the risk of FWDs snapping off at high  $\text{dv/dts}$ , causing the IGBT device in parallel with the FWD to turn back on due to the Miller capacitance effect.

#### 1.4-2 GATE DRIVE FAILURE PROBLEMS

Other important issues to consider are failure of the gate drive or the effect due to temporary loss of power. If the gate drive circuit fails it is helpful to have known fail safe condition. This can easily be achieved by introducing a resistor into the gate emitter connection that will discharge the gate emitter in the event of the gate drive losing power, (see fig.8).

The majority of problems with current sharing can be minimised by ensuring that the current paths to the individual modules are the same length and arranging the leads to equalise the effect of any mutual inductances between current paths to the individual paralleled modules.

 


Fig. 7 Circuit showing effect of parasites

 


Fig. 8 Circuit showing failsafe resistor

 
 


Fig. 9 Circuit showing simple method of supplying power via a transformer


**Fig. 10**

To damp these oscillations it can be helpful to place the gate resistor in the gate emitter connection to the IGBT rather than in the traditional gate connection (see fig 10).

## 2.0 DESCRIPTION OF THE GATE DRIVE AND IGBT TURN OFF WAVEFORMS

The turn off behaviour of an IGBT can be split into 4 phases as follows:

1. Gate is discharged until gate emitter voltage reaches the Miller plateau and the collector emitter voltage begins to rise slowly.
2. Collector-Emitter voltage rises quickly. The rate of rise of this voltage can be controlled by altering either the gate resistor or the gate turn off voltage. With a large resistor the rate of rise of voltage is very slow. If the gate resistance is reduced until the rate of voltage rise is limited by the rate of current rise then further reductions in  $R_g$  have no beneficial effect.
3. When the Collector-Emitter voltage has reached the DC link voltage the current in the IGBT falls rapidly. This rapid current fall causes an over voltage due to parasitic inductance in the circuit. An additional over shoot is caused by the VFR of the FWD diode turning on. The initial rate of fall of current is independent of the gate drive circuit if  $V_{ge}$  is below the threshold voltage, but it can be slowed if the gate emitter voltage is slightly above the threshold voltage at turn off. This however causes significant increase in switching losses and should only be used to remove fault conditions
4. The last stage of the turn off process is the decay of the tail current which cannot be controlled by the gate drive.

## POWER ASSEMBLY CAPABILITY

The Power Assembly group was set up to provide a support service for those customers requiring more than the basic semiconductor, and has developed a flexible range of heatsink and clamping systems in line with advances in device voltages and current capability of our semiconductors.

We offer an extensive range of air and liquid cooled assemblies covering the full range of circuit designs in general use today. The Assembly group offers high quality engineering support dedicated to designing new units to satisfy the growing needs of our customers.

Using the latest CAD methods our team of design and applications engineers aim to provide the Power Assembly Complete Solution (PACs).

## HEATSINKS

The Power Assembly group has its own proprietary range of extruded aluminium heatsinks which have been designed to optimise the performance of Dynex semiconductors. Data with respect to air natural, forced air and liquid cooling (with flow rates) is available on request.

For further information on device clamps, heatsinks and assemblies, please contact your nearest sales representative or Customer Services.



<http://www.dynexsemi.com>

e-mail: [power\\_solutions@dynexsemi.com](mailto:power_solutions@dynexsemi.com)

---

### HEADQUARTERS OPERATIONS

#### DYNEX SEMICONDUCTOR LTD

Doddington Road, Lincoln.  
Lincolnshire. LN6 3LF. United Kingdom.  
Tel: +44-(0)1522-500500  
Fax: +44-(0)1522-500550

### CUSTOMER SERVICE

Tel: +44 (0)1522 502753 / 502901. Fax: +44 (0)1522 500020

### SALES OFFICES

**Benelux, Italy & Switzerland:** Tel: +33 (0)1 64 66 42 17. Fax: +33 (0)1 64 66 42 19.

**France:** Tel: +33 (0)2 47 55 75 52. Fax: +33 (0)2 47 55 75 59.

**Germany, Northern Europe, Spain & Rest Of World:** Tel: +44 (0)1522 502753 / 502901.

Fax: +44 (0)1522 500020

**North America:** Tel: (613) 723-7035. Fax: (613) 723-1518. Toll Free: 1.888.33.DYNEX (39639) /  
Tel: (949) 733-3005. Fax: (949) 733-2986.

These offices are supported by Representatives and Distributors in many countries world-wide.  
© Dynex Semiconductor 2002 TECHNICAL DOCUMENTATION – NOT FOR RESALE. PRODUCED IN  
UNITED KINGDOM

---

### Datasheet Annotations:

Dynex Semiconductor annotate datasheets in the top right hand corner of the front page, to indicate product status. The annotations are as follows:-

**Target Information:** This is the most tentative form of information and represents a very preliminary specification. No actual design work on the product has been started.

**Preliminary Information:** The product is in design and development. The datasheet represents the product as it is understood but details may change.

**Advance Information:** The product design is complete and final characterisation for volume production is well in hand.

**No Annotation:** The product parameters are fixed and the product is available to datasheet specification.

---

This publication is issued to provide information only which (unless agreed by the Company in writing) may not be used, applied or reproduced for any purpose nor form part of any order or contract nor to be regarded as a representation relating to the products or services concerned. No warranty or guarantee express or implied is made regarding the capability, performance or suitability of any product or service. The Company reserves the right to alter without prior notice the specification, design or price of any product or service. Information concerning possible methods of use is provided as a guide only and does not constitute any guarantee that such methods of use will be satisfactory in a specific piece of equipment. It is the user's responsibility to fully determine the performance and suitability of any equipment using such information and to ensure that any publication or data used is up to date and has not been superseded. These products are not suitable for use in any medical products whose failure to perform may result in significant injury or death to the user. All products and materials are sold and services provided subject to the Company's conditions of sale, which are available on request.

All brand names and product names used in this publication are trademarks, registered trademarks or trade names of their respective owners.