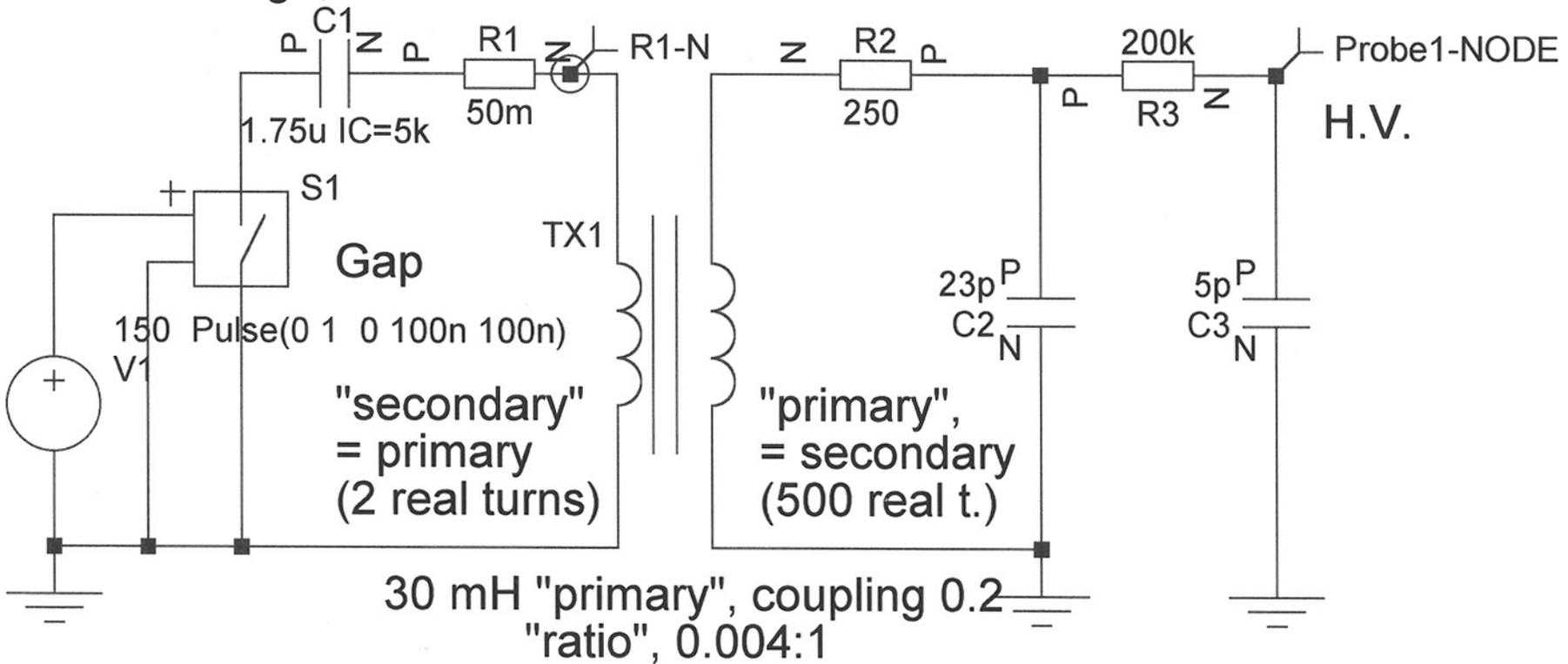


Initial charge, 5 KV

$f_r = \sim 164 \text{ KHz}$



Simulation of a conventional Tesla coil utilizing a reversed-transformer component. Ken Herrick 5/17/03.